Formula sheet: the triangle

Cover V for I x R. Cover I for V / R. Cover R for V / I. Two known values always give the third. MARKER-FORM-P1.

Symbols and units

symbol	quantity	unit
V	voltage	volts
I	current	amps
R	resistance	ohms (omega)

One-minute problems

given	find	answer
12V, 250 ohm	I	0.048 A = 48 mA
6V, 250 ohm	I	0.024 A = 24 mA
48mA, 250 ohm	V	12 V

Problem bank (20 drills)

n	given	find	answer
1	12V, 250 ohm	I	48.0 mA
2	6V, 250 ohm	I	24.0 mA
3	9V, 250 ohm	I	36.0 mA
4	3V, 250 ohm	I	12.0 mA
5	24V, 470 ohm	I	51.1 mA
6	9V, 100 ohm	I	90.0 mA
7	5V, 100 ohm	I	50.0 mA
8	12V, 100 ohm	I	120.0 mA
9	6V, 150 ohm	I	40.0 mA
10	9V, 150 ohm	I	60.0 mA
11	15V, 250 ohm	I	60.0 mA
12	7.5V, 250 ohm	I	30.0 mA
13	4.5V, 100 ohm	I	45.0 mA
14	10V, 470 ohm	I	21.3 mA
15	2.5V, 100 ohm	I	25.0 mA
16	20V, 470 ohm	I	42.6 mA
17	1.5V, 100 ohm	I	15.0 mA
18	11V, 250 ohm	I	44.0 mA
19	8V, 150 ohm	I	53.3 mA
20	13.5V, 470 ohm	I	28.7 mA